
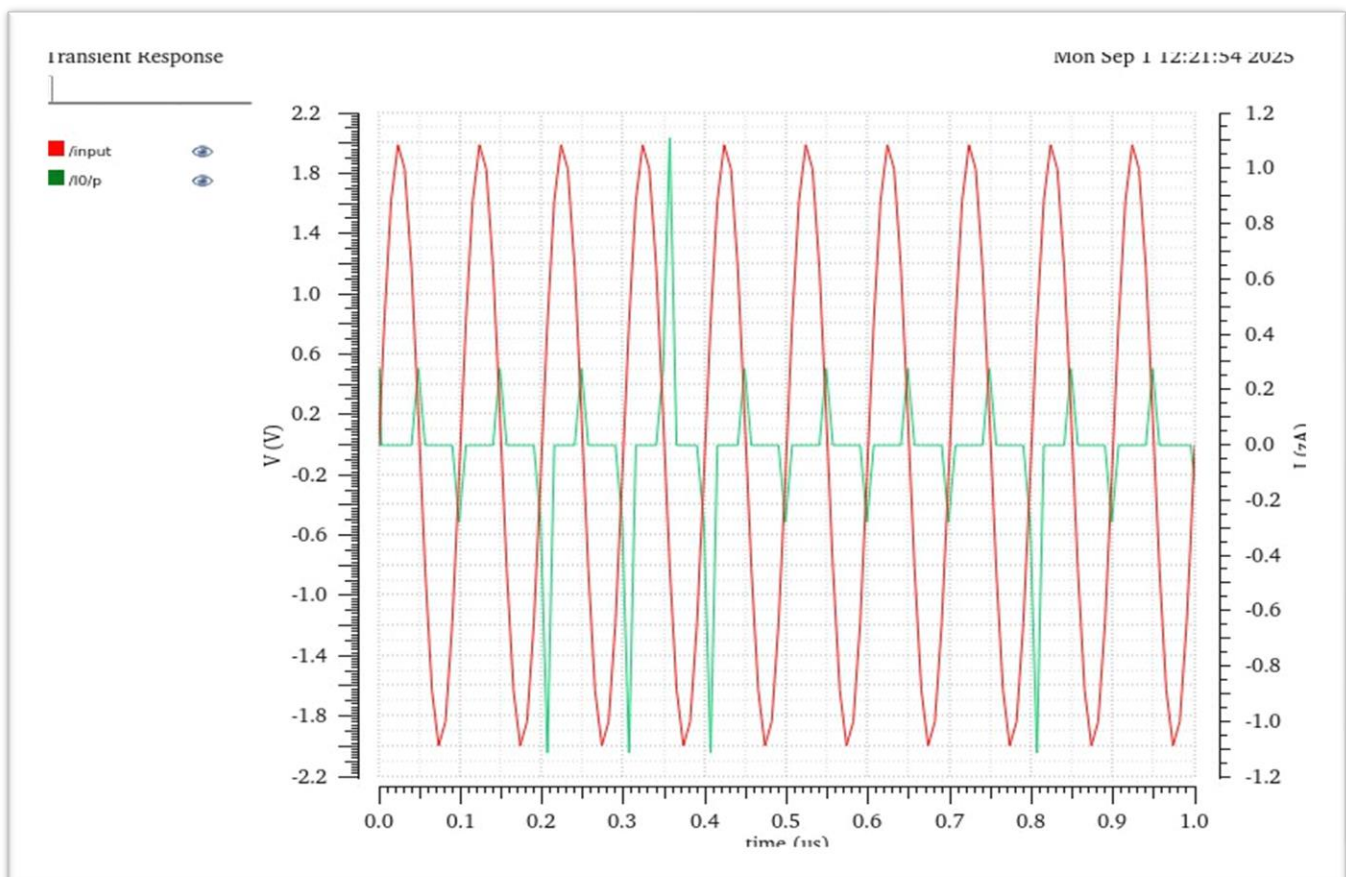



Name : Kushal kumar k (R24TL003)

Project Title : Implementation of threshold switching memristor in cadence.

➤ Cadence Output

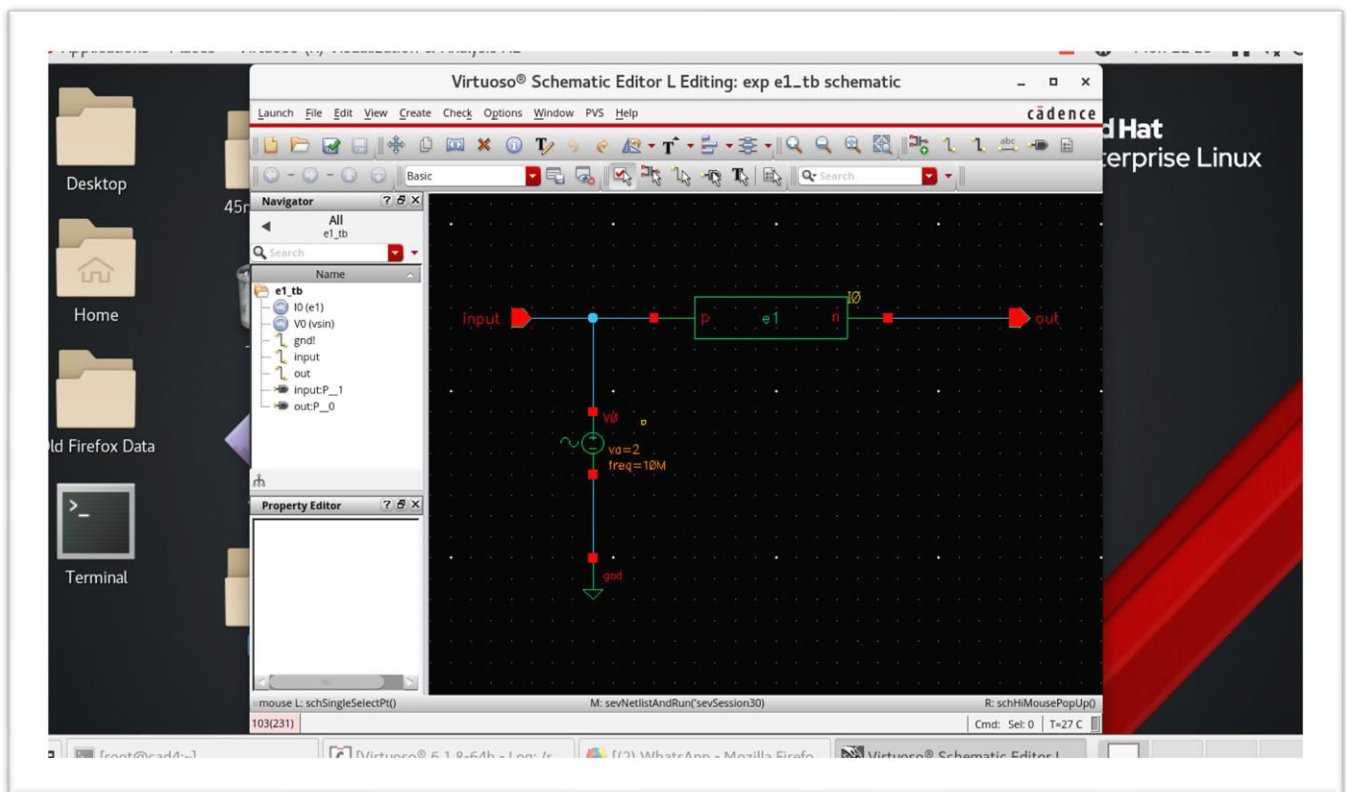

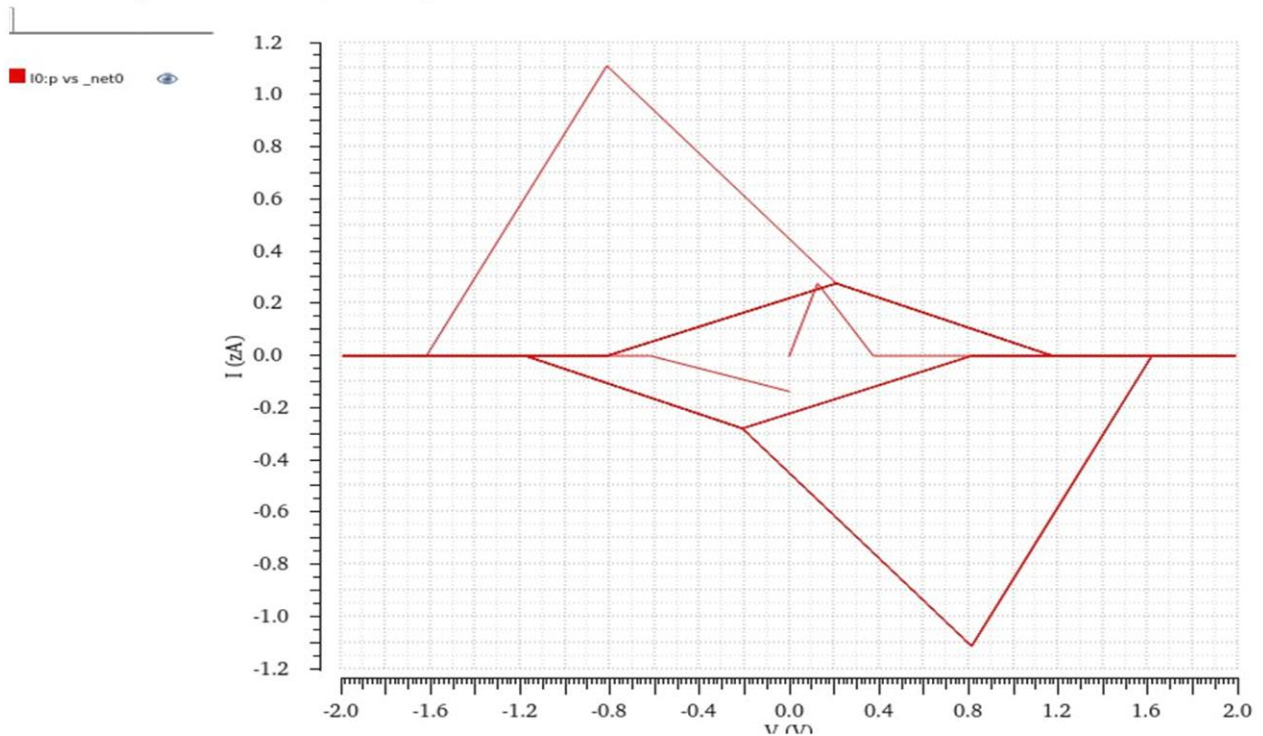Transient Analysis tran : time = (0 s -> 1 us)



➤ Matlab Output

